

Contents

1	Introduction	1
1.1	Power Amplifier as Part of a Transceiver System	2
1.2	Active and Passive Devices for Power Amplifier Design	3
1.3	Classification of Power Amplifiers	6
1.4	Basic Principles of Operation of Power Amplifiers	7
1.4.1	Power Amplifier Block Diagram	7
1.4.2	Output Power and Gain	8
1.4.3	Power Consumption	8
1.4.4	Power Efficiency	8
1.4.5	Output Power Capability	10
1.4.6	Maximum Operating Frequency of Power Amplifiers	10
1.4.7	Temperature Aspects of Power Amplifiers	11
1.4.8	Matching for Desired Power	11
1.4.9	Biasing	12
1.4.10	Conduction Angle	14
1.4.11	Distortion, Linearization and Increase of Power Output	14
1.4.12	Impact of Power Amplifier Turn-on Characteristics	15
1.4.13	Noise in Power Amplifiers	16
1.4.14	Measuring Large-Signal Power Amplifier Performance	16
1.4.15	Measuring Amplifier Power Gain and Stability	17
1.5	Justification for Computer-Aided Design	19
1.6	Organization of the Book	21
	References	23

Part I Power Amplifier Theory

2 Review of Telecommunication Aspects for Power Amplifier 29

Design 29

2.1 Wavelength and Transmission Bands 29

2.2 Review of Modulation Schemes 31

 2.2.1 Phase Shift-Keying 32

 2.2.2 Frequency Shift-Keying 32

 2.2.3 Phase-Amplitude Modulation 32

 2.2.4 Quadrature Amplitude Modulation 34

 2.2.5 On-Off Keying 34

 2.2.6 Orthogonal Frequency-Division Multiplexing 35

2.3 Antennas and Propagation 35

2.4 The Power Transistor 36

 2.4.1 Semiconductor Technologies for Transistor
 Fabrication 37

 2.4.2 Temperature Aspects of Transistors 39

 2.4.3 Transistor Models and Large-Signal Transistor
 Operation 41

2.5 Substrates for Discrete Implementations 44

2.6 The Smith Chart 45

2.7 Admittance (Y-) and Scattering (S-) Parameters 48

 2.7.1 Y-Parameters 48

 2.7.2 S-Parameters 50

 2.7.3 Conversion Between Y-Parameters
 and S-Parameters 52

2.8 Resonant Circuits 52

 2.8.1 Bandwidth 53

 2.8.2 Resonant Frequency 53

 2.8.3 Quality Factor 54

 2.8.4 Component Quality Factor 55

 2.8.5 Insertion Loss 55

 2.8.6 Coupling of Resonant Circuits 56

2.9 Fourier Analysis of Periodic Signals 57

2.10 Summary 59

References 59

3 Continuous-Mode Power Amplifiers 61

3.1 Class-A Power Amplifier 62

 3.1.1 Current and Voltage Waveform Analysis 64

 3.1.2 Power and Efficiency 65

 3.1.3 Bandwidth 68

 3.1.4 RFC and Coupling Capacitor 69

3.2	Class-B Power Amplifier.	69
3.2.1	Current and Voltage Waveform Analysis.	69
3.2.2	Power and Efficiency	70
3.3	Class-AB and Class-C Power Amplifiers.	73
3.3.1	Current and Voltage Waveform Analysis.	73
3.3.2	Power and Efficiency	76
3.4	Class-A/AB/B/C Power Amplifier	79
3.5	Push-Pull Class-A/AB/B/C Power Amplifier	80
3.5.1	Current and Voltage Waveform Analysis.	80
3.5.2	Power and Efficiency	82
3.6	Class-J Power Amplifiers	83
3.6.1	Current and Voltage Waveform Analysis.	84
3.6.2	Power and Efficiency	85
3.6.3	Calculating X_L	86
3.7	Doherty Power Amplifiers.	88
3.8	Recent State-of-the-Art Examples.	90
3.9	Summary	91
	References	91
4	Switch-Mode Power Amplifiers.	93
4.1	Class-D Power Amplifier.	94
4.1.1	Class-D Complementary Push-Pull Voltage-Switching Power Amplifier	94
4.1.2	Class-D Complementary Push-Pull Current-Switching Power Amplifier.	99
4.2	Class-E Power Amplifier.	103
4.2.1	Class-E Zero-Voltage-Switching Power Amplifier.	104
4.2.2	Class-E Zero-Current-Switching Power Amplifier.	111
4.2.3	Class-E ZVS Power Amplifier with Finite DC-Feed Inductance.	116
4.3	Class-F Power Amplifier.	118
4.3.1	Maximally Flat Class- F_3 Power Amplifier	119
4.3.2	Maximally Flat Class- F_{35} Power Amplifier	124
4.3.3	Maximally Flat Class- F_2 and Maximally Flat Class- F_{24} Power Amplifier (Class- F^{-1} Power Amplifiers)	128
4.3.4	Class-F Power Amplifier with Quarter-Wavelength Transmission Line	130
4.4	Other Power Amplifier Classes	133
4.5	Recent State-of-the-Art Examples.	133
4.6	Summary	134
	References	134

5	Passives for Power Amplifiers	137
5.1	Resistors	137
5.2	Capacitors	140
5.2.1	Discrete Capacitors	140
5.2.2	Integrated Capacitors	141
5.3	Inductors	143
5.3.1	Discrete Inductors	144
5.3.2	Integrated Active Inductors	148
5.3.3	Bond Wires	148
5.3.4	Spiral Inductors	149
5.3.5	MEMS Inductors	160
5.3.6	Other On-Chip Inductor Implementations	161
5.4	RF Chokes	162
5.5	Transformers	162
5.6	Quarter-Wavelength Transformer	162
5.6.1	General Transmission Line	164
5.6.2	Input Impedance of the Quarter-Wave Transformer	166
5.6.3	Bandwidth of the Quarter-Wave Transformer	166
5.6.4	Impedance of the Quarter-Wave Transformer Terminated with a Resonant Tank	168
5.7	Summary	169
	References	169
6	Impedance Matching	173
6.1	Importance of Impedance Matching	173
6.2	Load-Pull Characterization	174
6.3	Lumped-Element Matching	176
6.3.1	Wideband Two-Element Networks (L-Networks)	177
6.3.2	Narrowband Three-Element Networks (T- and Π -Networks)	180
6.4	Lumped Matching Using Smith Charts	183
6.5	Transmission-Line Impedance Matching	190
6.5.1	Variations of Transmission-Line Matching Networks	191
6.5.2	Quarter-Wave Transformer Impedance Matching	192
6.6	Impedance Matching Using MATLAB	193
6.7	Summary	194
	References	194

Part II Developing EDA for Power Amplifier Design

7	Intelligent Automated Design Ideas for Inductor Synthesis	199
7.1	Design of Integrated Inductors	199
7.1.1	Cut-and-Try Approach	200
7.1.2	Synthesis Approach	201

7.1.3	MEMS Inductors	214
7.1.4	Integrated Transformers.	218
7.1.5	Verification of the Inductor Model and the Search Algorithm	218
7.2	Bond Wires	223
7.2.1	Model.	224
7.2.2	Equations	224
7.2.3	Input Parameters	224
7.2.4	Development of the Inductor Design Routine.	226
7.2.5	Design Outputs	228
7.3	Discrete Inductors	228
7.4	Design Examples	230
7.5	Summary	234
	References	234
8	Full Power Amplifier System Design	235
8.1	Subroutine for Design of Class-E Zero-Voltage-Switching Power Amplifiers	236
8.1.1	Equations	236
8.1.2	Input Parameters	237
8.1.3	Description of the Subroutine.	238
8.1.4	Subroutine Outputs.	238
8.2	Subroutine for Design of the Class-F Power Amplifiers.	239
8.2.1	Equations	242
8.2.2	Input Parameters	243
8.2.3	Description of the Subroutine.	244
8.2.4	Subroutine Outputs.	244
8.3	Subroutine for Design of Class-F Power Amplifiers with Quarter-Wave Transmission Line	244
8.3.1	Equations	246
8.3.2	Input Parameters	247
8.3.3	Description of the Subroutine.	248
8.3.4	Subroutine Outputs.	249
8.4	Subroutine for Design of Class-A/AB/B/C Power Amplifiers	249
8.4.1	Equations	251
8.4.2	Input Parameters	253
8.4.3	Description of the Subroutine.	253
8.4.4	Subroutine Outputs.	254
8.5	Subroutine for Design of the Class-J Power Amplifiers	254
8.5.1	Equations	257
8.5.2	Input Parameters	257
8.5.3	Description of the Subroutine.	258
8.5.4	Subroutine Outputs.	258

8.6	Subroutine for Impedance Matching	260
8.6.1	Input Parameters	260
8.6.2	Subroutine Outputs	261
8.6.3	Equations	261
8.6.4	Description of the Subroutine.	261
8.7	Complete System Integration	263
8.7.1	Input Parameters	263
8.7.2	Routine Outputs	266
8.7.3	Description and Flow Diagram of the Power Amplifier Design Routine	268
8.7.4	MATLAB Code	270
8.8	Design Examples	270
8.9	Summary	305
	References	308
9	Practical Considerations of Integrated and Discrete Power Amplifier Solutions.	309
9.1	Practical Considerations Common to Integrated, Discrete and Hybrid (System-on-Package) Solutions	309
9.1.1	Gain of the Power Transistor	309
9.1.2	Component Loss	310
9.1.3	Feasibility of Component Values	311
9.1.4	Influence of the Frequency and the Wavelength	312
9.1.5	Coupling	312
9.2	Integrated Circuit Considerations	313
9.2.1	Design Rule Checks and Technology Considerations	313
9.2.2	Extraction of a Spiral Inductor Layout into a GDSII File	313
9.2.3	Bond-Pad Considerations	314
9.2.4	Bond-Wire Considerations	314
9.2.5	Package Lead Considerations	319
9.3	Systems-on-Package Considerations	321
9.4	From Theoretical Design Using Custom EDA to Practical Design	325
9.5	Summary	328
	References	328
10	Future Directions and Final Remarks	331
10.1	Power Amplifiers Utilizing Transmission Lines	331
10.1.1	Class-E Power Amplifier Utilizing Transmission Lines	332
10.1.2	Class-F Power Amplifier Utilizing Transmission Lines	334

10.2 Near-Terahertz Frequencies 335

10.3 Other Design Automation Ideas and Ideas for Expansion
of Devised Programs 336

10.4 Final Remarks 337

References 337



<http://www.springer.com/978-3-319-28375-3>

Power Amplifiers for the S-, C-, X- and Ku-bands
An EDA Perspective

Božanić, M.; Sinha, S.

2016, XIX, 337 p. 305 illus. in color., Hardcover

ISBN: 978-3-319-28375-3