

Contents

1	Introduction	1
1.1	Typical Structure and Equivalent Circuits of Power Supply Systems. Features of Circuits with Variable Operating Regime Parameters	1
1.2	Disadvantages of the Well-Known Calculation Methods of Regime Parameters in the Relative Form for Active Two-Poles	3
1.2.1	Volt–Ampere Characteristics of an Active Two-Pole	3
1.2.2	Regime Parameters in the Relative Form	4
1.2.3	Regime Change in the Relative Form	7
1.2.4	Active Two-Port with Changeable Resistance	9
1.2.5	Scales of Regime Parameters for Cascaded Two-Ports	9
1.3	Analysis of the Traditional Approach to Normalizing of Regime Parameters for the Voltage Linear Stabilization	11
1.4	Active Two-Port	14
1.4.1	Volt Characteristics of an Active Two-Port	14
1.4.2	Traditional Recalculation of the Load Currents.	14
1.5	Nonlinear Characteristics	17
1.5.1	Efficiency of Two-Ports with Different Losses	17
1.5.2	Characteristic Regimes of Solar Cells	20
1.5.3	Quasi-resonant Voltage Converter.	20
1.5.4	Power-Source and Power-Load Elements.	21
1.6	Regulated Voltage Converters	21
1.6.1	Voltage Regulator with a Limited Capacity Voltage Source	21
1.6.2	Buck Converter	23
1.6.3	Boost Converter.	24
	References	25

Part I Electrical Circuits with one Load. Projective Coordinates of a Straight Line Point

2	Operating Regimes of an Active Two-Pole. Display of Projective Geometry.	29
2.1	Volt–Ampere Characteristics of an Active Two-Pole. Affine and Projective Transformations of Regime Parameters	29
2.1.1	Affine Transformations	29
2.1.2	Projective Transformations	37
2.2	Volt–Ampere Characteristics of an Active Two-Pole with a Variable Element	42
2.2.1	Thévenin Equivalent Circuit with the Variable Internal Resistance	42
2.2.2	Norton Equivalent Circuit with the Variable Internal Conductivity	44
2.3	Regime Symmetry for a Load-Power	47
2.3.1	Symmetry of Consumption and Return of Power	48
2.3.2	Symmetry Relatively to the Maximum Power Point	50
2.3.3	Two Systems of Characteristic Points	52
	References	54
3	Generalized Equivalent Circuit of an Active Two-Pole with a Variable Element.	55
3.1	Introduction.	55
3.2	Circuit with a Series Variable Resistance.	56
3.2.1	Disadvantage of the Known Equivalent Circuit	56
3.2.2	Generalized Equivalent Circuit.	57
3.2.3	Relative Operative Regimes. Recalculation of the Load Current	60
3.2.4	Example	65
3.3	Circuit with a Shunt Variable Conductivity	70
3.3.1	Disadvantage of the Known Equivalent Circuit	70
3.3.2	Generalized Equivalent Circuit.	71
3.3.3	Relative Operative Regimes. Recalculation of the Load Current	74
3.3.4	Example	78
3.4	General Case of an Active Two-Pole with a Variable Conductivity	82
3.4.1	Known Equivalent Generator.	83
3.4.2	Generalized Equivalent Circuit.	84
3.4.3	Example of a Circuit. Recalculation of the Load Current	87
3.5	Stabilization of the Load Current	91
	References	94

4	Two-Port Circuits	97
4.1	Input-Output Conformity of Two-Ports as Affine Transformations	97
4.1.1	Conformity of a Two-Port	97
4.1.2	Conformity of Cascaded Two-Ports	99
4.2	Input-Output Conformity of Two-Ports as Projective Transformations	102
4.2.1	Conformity of a Two-Port	102
4.2.2	Versions of Conformities, Invariants, and Cross Ratios	106
4.2.3	Conformity of Cascaded Two-Ports	109
4.3	Use of Invariant Properties for the Transfer of Measuring Signals	116
4.3.1	Transfer of Signals over an Unstable Two-Port	116
4.3.2	Conductivity Measurement by an Unstable Two-Port	119
4.4	Deviation from the Maximum Efficiency of a Two-Port	120
4.4.1	Regime Symmetry for the Input Terminals	121
4.4.2	Regime Symmetry for the Output or Load	123
4.5	Effectiveness of Modular Connections	126
4.5.1	Complementary Knowledge About a Two-Port	126
4.5.2	Parallel Connection of Two Converters	127
4.5.3	Connection of Two-Ports with the Interaction	130
4.6	Effectiveness Indices of a Two-Port with Variable Losses	131
4.6.1	Problems of Energy Indices	131
4.6.2	Influence of Losses on the Load Power	131
4.6.3	Influence of Losses on the Efficiency	135
	References	138
5	Paralleling of Limited Capacity Voltage Sources	141
5.1	Introduction	141
5.2	Initial Relationships	141
5.3	Influence of the Load Value on the Current Distribution	143
5.3.1	Analysis of Paralleling Voltage Sources	143
5.3.2	Introduction of Two Concepts	145
5.3.3	Comparison of a Loading Regime of Different Circuits	148
5.4	Influence of the Equalizing Resistance on the Current Distribution	153
5.4.1	Analysis of Paralleling Voltage Sources	153
5.4.2	Introduction of Two Concepts	154
5.4.3	Comparison of a Loading Regime of Different Circuits	157
	References	162

Part II Multi-port Circuits. Projective Coordinates of a Point on the Plane and Space

6	Operating Regimes of an Active Multi-port	167
6.1	Active Two-Port. Affine and Projective Coordinates on the Plane	167
6.1.1	Affine Coordinates	167
6.1.2	Particular Case of a Two-Port. Introduction of the Projective Plane	173
6.1.3	General Case of a Two-Port. Projective Coordinates	175
6.2	Projective Coordinates in Space	183
6.2.1	Particular Case of a Multi-port	183
6.2.2	General Case of a Multi-port. The Balanced Networks	190
6.3	Projective Coordinates of an Active Two-Port with Stabilization of Load Voltages	198
	References	205
7	Recalculation of Load Currents of Active Multi-ports	207
7.1	Recalculation of Currents for the Case of Load Changes	207
7.1.1	Active Two-Port	207
7.1.2	Active Three-Port	210
7.2	Recalculation of Currents for the Case of Changes of Circuit Parameters	213
7.2.1	Change of Lateral Conductivity	213
7.2.2	Change of Longitudinal Conductivity	219
7.3	Comparison of Regimes and Parameters of Active Two-Ports	224
7.4	Comparison of Regime of Active Two-Ports with Linear Stabilizations of Load Voltages	228
	References	235
8	Passive Multi-port Circuits	237
8.1	Input-Output Conformity of Four-Ports as an Affine Transformation	237
8.2	Input-Output Conformity of Four-Ports as a Projective Transformation	244
8.2.1	Output of a Four-Port	244
8.2.2	Input of a Four-Port	246
8.2.3	Recalculation of Currents at Load Changes	251
8.2.4	Two Cascaded Four-Port Networks	252
8.2.5	Examples of Calculation	254
8.3	Transmission of Two Signals Over Three-Wire Line	260
8.3.1	Transmission by Using of Cross-Ratio	260
8.3.2	Transmission by Using of Affine Ratio	262

8.4 Input-Output Conformity of a Balanced Six-Port 263

References 273

9 Generalized Equivalent Circuit of a Multi-port 275

9.1 Generalized Equivalent of an Active Two-Port. 275

9.1.1 Disadvantages of Known Equivalent. 275

9.1.2 Introduction of the Formal Variant
of a Generalized Equivalent. 276

9.1.3 Introduction of the Principal Variant
of a Generalized Equivalent Circuit 279

9.2 Generalized Equivalent of an Active Three-Port. 282

References 286

Part III Circuits with Non-Linear Regulation Curves

10 Regulation of Load Voltages. 289

10.1 Base Model. Display of Conformal Geometry 289

10.2 Using of Hyperbolic Geometry Model 295

10.2.1 Case of One Load 296

10.2.2 Case of Two Loads 299

10.3 Example 305

10.3.1 Case of One Load 306

10.3.2 Case of Two Loads 308

References 312

11 Stabilization of Load Voltages 313

11.1 Analysis of Load Voltage Stabilization Regimes 313

11.1.1 Case of One Load 313

11.1.2 Use of Hyperbolic Geometry 315

11.1.3 Case of Two Loads 322

11.2 Given Voltage for the First Variable Load and Voltage
Regulation of the Second Given Load. 324

11.2.1 Use of Hyperbolic Geometry 328

11.2.2 Regime Change for the First Given
Load Resistance. 330

11.2.3 Example 333

References 334

12 Pulse-Width Modulation Regulators 337

12.1 Introduction. 337

12.2 Regulation Characteristic of Boost Converter. 337

12.3 Regulation Characteristic of Buck–Boost Converter 348

12.3.1 Buck–Boost Converter with an Idealized Choke. 348

12.3.2 Buck–Boost Converter with Losses of Choke 354

References 357

Part IV Circuits with Non-Linear Load Characteristics

13 Power-Source and Power-Load Elements 361

13.1 Introduction. 361

13.2 Two-Valued Regime of a Regulated Converter.
The Concept of a Power-Source and Power-Load Element 361

13.3 Influence of Voltage Source Parameters and Power-Load
Element onto a Power Supply Regime 363

13.3.1 Ideal Voltage Source 363

13.3.2 Voltage of a Power Supply with Limited Capacity 364

13.3.3 Internal Resistance of a Voltage Source 370

13.3.4 Power of a Power-Load Element 372

13.4 Power-Load Element with Losses. 374

13.4.1 Series Loss Resistance 374

13.4.2 Two-Port Loss Circuit. 375

13.5 Power Supply Line with Losses. 381

References 388

**14 Quasi-resonant Voltage Converter with Self-limitation
of Load Current. Similarity of Load Characteristics
of Some Electronic Devices** 389

14.1 Load Curve of an Active Two-Pole with Self-limitation
of the Current 389

14.2 Equivalent Generator of an Active Two-Pole
with Self-limitation of Current. 392

14.3 Deviation from the Maximum Load Power Point 396

14.4 Symmetrical Load Characteristic for the Full Area of the Load
Voltage Variation. 400

14.5 Asymmetrical Load Characteristics. 401

14.6 Linearly Hyperbolic Approximation of a Solar Cell
Characteristic. 405

14.6.1 Approximation Problem 405

14.6.2 Formal Linearly Hyperbolic Approximation. 405

References 410

Conclusions 413

Index 415



<http://www.springer.com/978-3-319-28450-7>

Analysis of Electrical Circuits with Variable Load Regime
Parameters

Projective Geometry Method

Penin, A.

2016, XXI, 417 p. 269 illus., Hardcover

ISBN: 978-3-319-28450-7