

Contents

1. INTRODUCTION	1
1 The pioneers of wireless communication	1
2 Evolution of awareness of electromagnetic compatibility	3
3 Electromagnetic compatibility of integrated circuits	5
4 Scope of this book	7
2. BASIC EMC CONCEPTS AT IC LEVEL	11
1 Introduction	11
2 Definition of EMC, EMI, EMS and EME	12
3 Sources of electromagnetic interference	14
4 Electromagnetism versus integrated circuit design	15
4.1 Electrical length	15
4.2 Near field versus far field	17
4.3 Radiation of a conductor	19
4.4 Basic EMC antenna concepts	20
4.5 Radiated, induced and conducted disturbances	22
4.6 Practical example	24
5 Intra-chip versus externally-coupled EMC	27
6 Analog versus digital integrated circuits	29
7 EMC in automotive applications	31
8 Immunity measurement methods for IC's: IEC 62132	31

3.	EMC OF INTEGRATED CIRCUITS VERSUS DISTORTION	37
1	Introduction	37
2	Relationship between EMI resisting design and distortion	39
2.1	Linear distortion	39
2.2	Nonlinear distortion (rectification)	40
2.3	Weak and strong nonlinear distortion	43
3	Case study 1: diode connected NMOS transistor	45
4	Case study 2: NMOS source follower	50
5	Case study 3: NMOS current mirror	52
5.1	Capacitor decoupling the mirror node	57
5.2	Low-pass R - C filter in the mirror node	58
5.3	Low-pass R - C filter in the drain of M_1	60
5.4	EMI resisting (4-transistor) current mirror	61
5.5	EMI resisting (Wilson totem pole) current mirror	67
5.6	Comparison of EMI susceptibility of current mirrors	69
6	Case study 4: EMI susceptibility in ESD protections	72
6.1	Weak nonlinear distortion in ESD protections	73
6.2	Strong nonlinear distortion in ESD protections	78
6.3	ESD protections: general conclusions	80
7	EMI induced DC shift	81
4.	EMI RESISTING ANALOG OUTPUT CIRCUITS	83
1	Introduction	83
2	Categorization of analog output structures	85
2.1	Common-drain output circuits	85
2.2	Common-source output circuits	88
2.3	Comparing the electromagnetic susceptibility	89
2.4	Large EMI amplitudes	93
3	Case study 1: EMI resisting DC current regulator	95
3.1	EMI issues in a classic DC current regulator	95
3.1.1	EMI issues: small signal analysis	97
3.1.2	EMI issues: large signal analysis	99
3.1.3	Decoupling capacitor C_d	100
3.2	DC current regulator with a high immunity to EMI	102
3.3	Measurements	106

4	Case study 2: EMI resisting LIN driver	107
4.1	Classic LIN driver	111
4.1.1	Linear operation mode	114
4.1.2	Nonlinear operation mode	116
4.2	EMI resisting LIN driver topology: LIN driver 1	117
4.2.1	EMI path 1	118
4.2.2	EMI path 2	122
4.2.3	Slope control function	129
4.2.4	Measurements	129
4.3	EMI resisting LIN driver topology: LIN driver 2	133
4.3.1	Smart-power mode	133
4.3.2	Slope pumping reduction	136
4.3.3	Measurements	138
5.	EMI RESISTING ANALOG INPUT CIRCUITS	141
1	Introduction	141
2	Case study 1: electromagnetic immunity of CMOS operational amplifiers	142
2.1	Asymmetric slew rate	145
2.2	Strong nonlinear behavior of the input differential pair	148
2.3	Weak nonlinear behavior of the input differential pair	149
2.3.1	EMI induced offset in a classic differential pair	149
2.3.2	Classic differential pair using source degeneration	154
2.3.3	Cross-coupled differential pair	155
2.3.4	Differential pair with low-pass R - C filter	158
2.3.5	Improved cross-coupled differential pair	160
2.3.6	Source-buffered differential pair	161
2.3.7	Comparison	169
2.4	EMI induced offset measurement setups	169
2.5	Measurements	177
3	Case study 2: EMI resisting instrumentation amplifier input circuit	182
3.1	Classic instrumentation amplifier input circuit	183
3.2	Input circuit using current sources modulation	189
3.3	Simulations	193

6. EMI RESISTING BANDGAP REFERENCES AND LOW DROPOUT VOLTAGE REGULATORS	197
1 Introduction	197
2 Case study 1: CMOS bandgap voltage references with a high immunity to EMI	201
2.1 EMI injection in a Kuijk bandgap reference (NPD)	202
2.1.1 Small signal analysis	205
2.1.2 Large signal analysis	206
2.2 EMI resisting Kuijk bandgap reference (PPD)	208
2.2.1 Small signal analysis	210
2.2.2 Large signal analysis	211
2.3 EMI resisting Kuijk bandgap reference (PPDAL)	211
2.3.1 Small signal analysis	213
2.3.2 Large signal analysis	214
2.4 Startup circuit and biasing	215
2.5 Measurements	215
3 Case study 2: EMI resisting low dropout voltage regulators	220
3.1 EMI issues in LDO voltage regulator circuits	220
3.2 Design example	226
7. EPILOGUE	227
REFERENCES	231
INDEX	241



<http://www.springer.com/978-90-481-3229-4>

EMC of Analog Integrated Circuits

Redouté, J.-M.; Steyaert, M.

2010, X, 243 p., Hardcover

ISBN: 978-90-481-3229-4