

# Contents

- Preface ..... xi
- Symbols ..... xiii
- 1 Introduction** ..... 1
  - 1.1 Applications of Quartz Crystal Oscillators ..... 1
  - 1.2 Historical Notes ..... 2
  - 1.3 The Book Structure ..... 2
  - 1.4 Basics on Oscillators ..... 4
- 2 Quartz and MEM Resonators** ..... 7
  - 2.1 The Quartz Resonator ..... 7
  - 2.2 Equivalent Circuit ..... 8
  - 2.3 Figure of Merit ..... 10
  - 2.4 Mechanical Energy and Power Dissipation ..... 15
  - 2.5 Various Types of Quartz Resonators ..... 15
  - 2.6 MEM Resonators ..... 18
    - 2.6.1 Basic Generic Structure ..... 18
    - 2.6.2 Symmetrical Transducers ..... 21
- 3 General Theory of High-Q Oscillators** ..... 23
  - 3.1 General Form of the Oscillator ..... 23
  - 3.2 Stable Oscillation ..... 25
  - 3.3 Critical Condition for Oscillation and Linear Approximation . 27
  - 3.4 Amplitude Limitation ..... 27
  - 3.5 Start-up of Oscillation ..... 29
  - 3.6 Duality ..... 30
  - 3.7 Basic Considerations on Phase Noise ..... 31
    - 3.7.1 Linear Circuit ..... 31

- 3.7.2 Nonlinear Time Variant Circuit ..... 33
- 3.8 Model of the MOS Transistor ..... 36
- 4 Theory of the Pierce Oscillator ..... 41**
  - 4.1 Basic Circuit ..... 41
  - 4.2 Linear Analysis ..... 42
    - 4.2.1 Linearized Circuit ..... 42
    - 4.2.2 Lossless Circuit ..... 46
    - 4.2.3 Phase Stability ..... 50
    - 4.2.4 Relative Oscillator Voltages ..... 51
    - 4.2.5 Effect of Losses ..... 52
    - 4.2.6 Frequency Adjustment ..... 54
  - 4.3 Nonlinear Analysis ..... 55
    - 4.3.1 Numerical Example ..... 55
    - 4.3.2 Distortion of the Gate Voltage ..... 57
    - 4.3.3 Amplitude Limitation by the Transistor Transfer Function ..... 58
    - 4.3.4 Energy and Power of Mechanical Oscillation ..... 68
    - 4.3.5 Frequency Stability ..... 69
    - 4.3.6 Elimination of Unwanted Modes ..... 71
  - 4.4 Phase Noise ..... 77
    - 4.4.1 Linear Effects on Phase Noise ..... 77
    - 4.4.2 Phase Noise in the Nonlinear Time Variant Circuit .... 78
  - 4.5 Design Process ..... 84
    - 4.5.1 Design Steps ..... 84
    - 4.5.2 Design Examples ..... 89
- 5 Implementations of the Pierce Oscillator ..... 93**
  - 5.1 Grounded-Source Oscillator ..... 93
    - 5.1.1 Basic Circuit ..... 93
    - 5.1.2 Dynamic Behavior of Bias ..... 95
    - 5.1.3 Dynamic Behavior of Oscillation Amplitude ..... 97
    - 5.1.4 Design Examples ..... 100
    - 5.1.5 Implementation of the Drain-to-Gate Resistor ..... 102
    - 5.1.6 Increasing the Maximum Amplitude ..... 106
  - 5.2 Amplitude Regulation ..... 107
    - 5.2.1 Introduction ..... 107
    - 5.2.2 Basic Regulator ..... 108
    - 5.2.3 Amplitude Regulating Loop ..... 115
    - 5.2.4 Simplified Regulator Using Linear Resistors ..... 118

- 5.2.5 Elimination of Resistors . . . . . 120
- 5.3 Extraction of the Oscillatory Signal . . . . . 123
- 5.4 CMOS-Inverter Oscillator . . . . . 124
  - 5.4.1 Direct Implementation . . . . . 124
  - 5.4.2 Current-controlled CMOS-inverter oscillator. . . . . 129
- 5.5 Grounded-Drain Oscillator . . . . . 132
  - 5.5.1 Basic Implementation . . . . . 132
  - 5.5.2 Single-Substrate Implementation . . . . . 133
- 6 Alternative Architectures . . . . . 137**
  - 6.1 Introduction . . . . . 137
  - 6.2 Symmetrical Oscillator for Parallel Resonance . . . . . 137
    - 6.2.1 Basic Structure . . . . . 137
    - 6.2.2 Linear Analysis with the Parallel Resonator . . . . . 139
    - 6.2.3 Linear Analysis with the Series Motional Resonator . . 140
    - 6.2.4 Effect of Losses . . . . . 143
    - 6.2.5 Nonlinear Analysis . . . . . 144
    - 6.2.6 Phase Noise . . . . . 149
    - 6.2.7 Practical Implementations . . . . . 157
  - 6.3 Symmetrical Oscillator for Series Resonance . . . . . 164
    - 6.3.1 Basic Structure . . . . . 164
    - 6.3.2 Linear Analysis . . . . . 165
    - 6.3.3 Nonlinear Analysis . . . . . 172
    - 6.3.4 Phase Noise . . . . . 177
    - 6.3.5 Practical Implementation . . . . . 183
  - 6.4 Van den Homberg Oscillator . . . . . 190
    - 6.4.1 Principle and Linear Analysis . . . . . 190
    - 6.4.2 Practical Implementation and Nonlinear Behavior . . . 193
  - 6.5 Comparison of Oscillators . . . . . 194
    - 6.5.1 Pierce Oscillator (1) . . . . . 195
    - 6.5.2 Van den Homberg Oscillator (2) . . . . . 196
    - 6.5.3 Parallel Resonance Oscillator (3) . . . . . 196
    - 6.5.4 Series Resonance Oscillator (4) . . . . . 197
- Bibliography . . . . . 201**
- Index . . . . . 203**



<http://www.springer.com/978-90-481-9394-3>

Low-Power Crystal and MEMS Oscillators  
The Experience of Watch Developments  
Vittoz, E.

2010, XVIII, 206 p., Hardcover

ISBN: 978-90-481-9394-3